
Pipelining and Parallel Processing


1-Stage (non-pipelined)

$$y_i = (m_i \times x_i) + c_i$$

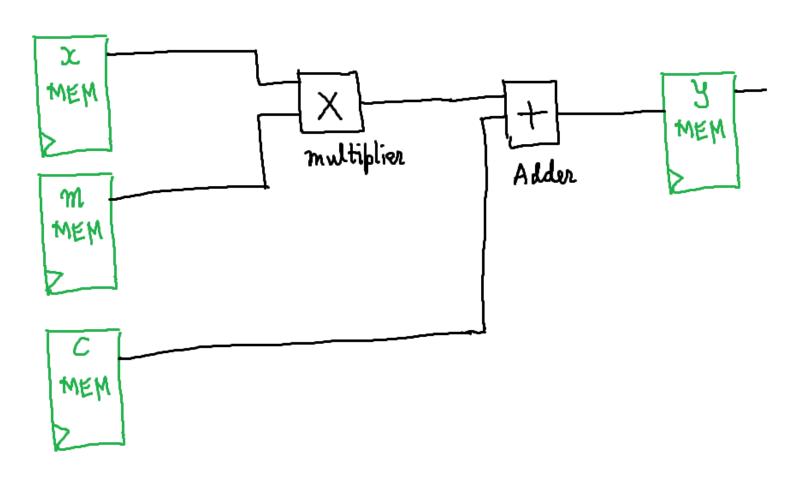


Decompose into more stages: How?

$$y_i = (m_i \times x_i) + c_i$$

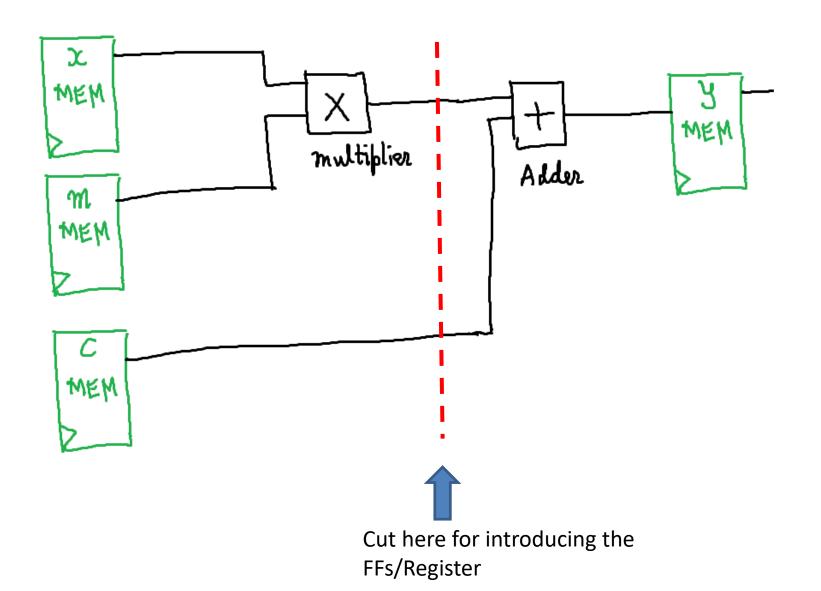

2-Stage Pipelined

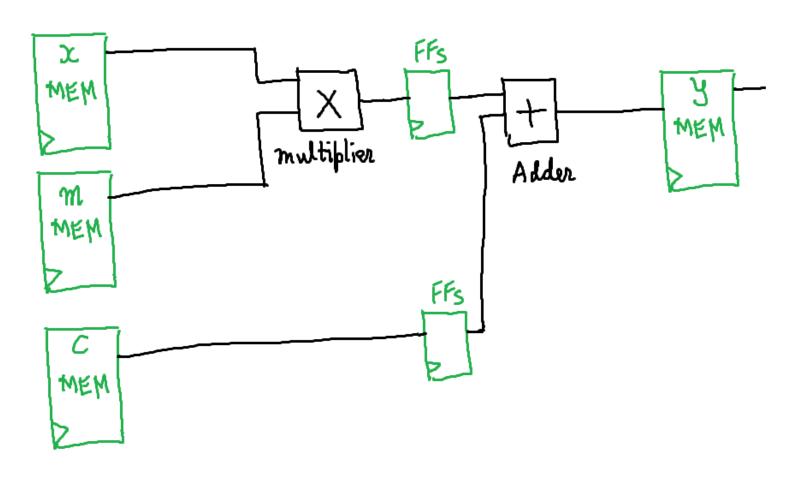
$$\mathbf{y}_i = (\mathbf{m}_i \times \mathbf{x}_i) + \mathbf{c}_i$$



We want to implement

 $y_i = (m_i \times x_i) + c_i$

Un-pipelined design (1 stage design)

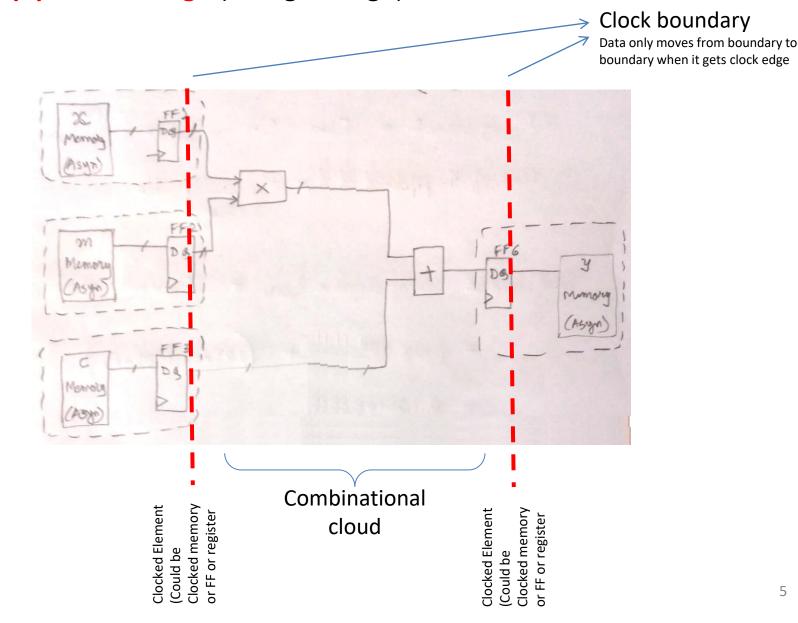


We want to implement

 $y_i = (m_i \times x_i) + c_i$

Pipelined design (2 stage design)

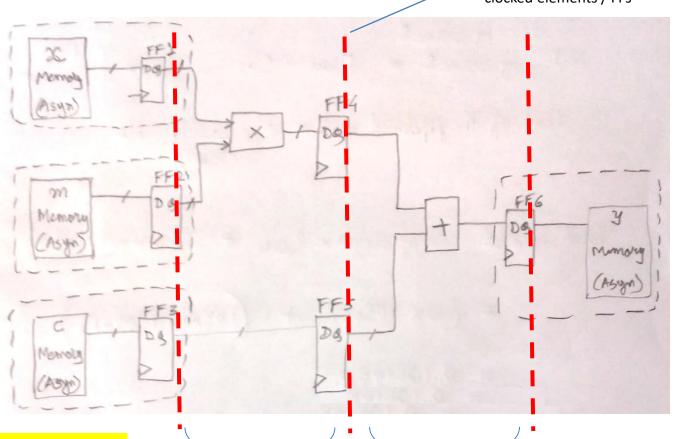We have deliberately cut the large combinational cloud into two by inserting this clocked elements / FFs



Clocked Element


See the solved numerical related to this diagram in next few slides...

Combinational cloud Stage-1

Combinational cloud Stage-2

Clocked Element

6

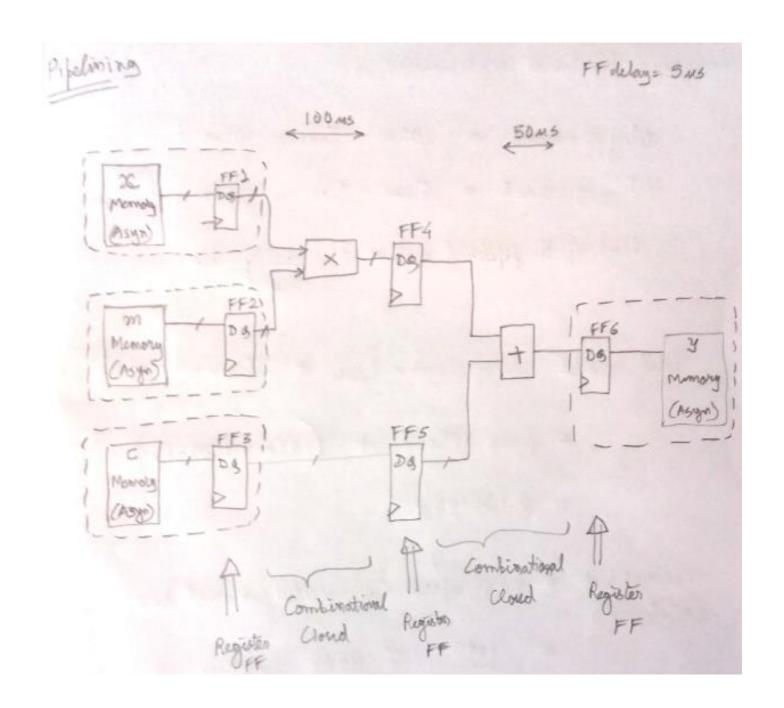

Lets say we have to do 1000 (y=mx+c) operations. Whitelined vousion: Delay = 100MS+ 50MS = 150 MS means for Combinational Cloud I stage design delay = 150 ms + 5 ms = 155 ms Total delay = 155 ms x 1000 = 0.155 s

